

Circuit Demonstration Page

Student names: Maya Martin Xingpeng Li

Instructor Initials

Pushbutton "Or Gate"

MP

Transistor Not gate

MP

Transistor Nor gate

MP


Transistor unknown gate

MP


Diagrams

On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.

Inverter:

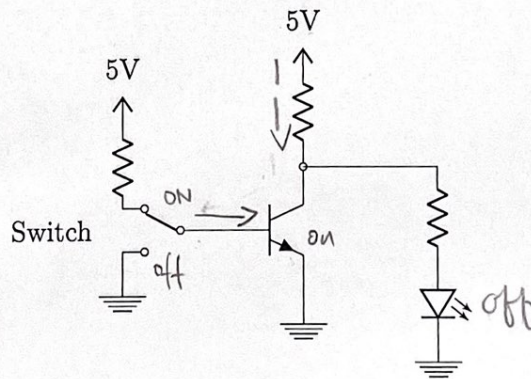

NOR:

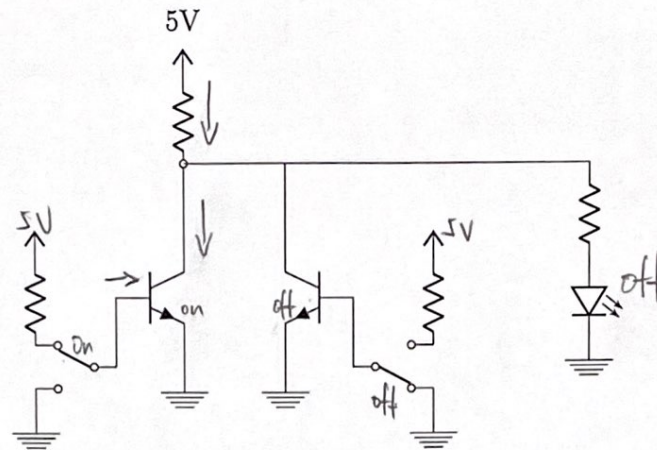

Final gate:

